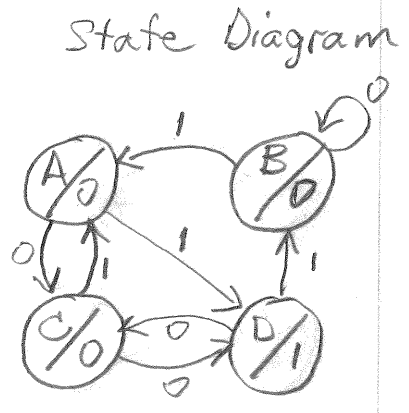


Finite State Machine (FSM) Design

Given the following State/Output Table/Diagram design a FSM with D flip-flops

Current State <u>S</u>	Next State		Output <u>Z</u>
	<u>W=0</u>	<u>W=1</u>	
A	C	D	0
B	B	A	0
C	D	A	0
D	C	B	1




using the Simplest State assignment (binary order) requires two flip-flops. The Transition-Output Table is

Current State		Next State		Output <u>Z</u>
<u>Q1</u>	<u>Q2</u>	<u>W=0</u>	<u>W=1</u>	
0	0	1	0	0
0	1	0	1	0
1	0	1	1	0
1	1	1	0	1


$Q1^* \quad Q2^* \quad Q1^* \quad Q2^*$

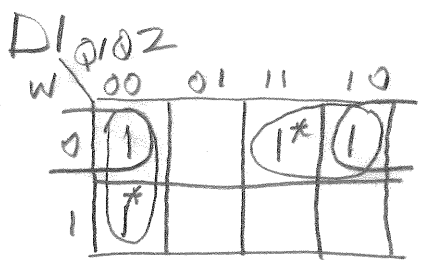Since the Characteristic equation for a D flip-flop is $Q^* = D$, the Excitation \equiv Transition Table. The K-maps for the excitation equation are



$$D1 = Q1' \cdot Q2' + Q1 \cdot W'$$
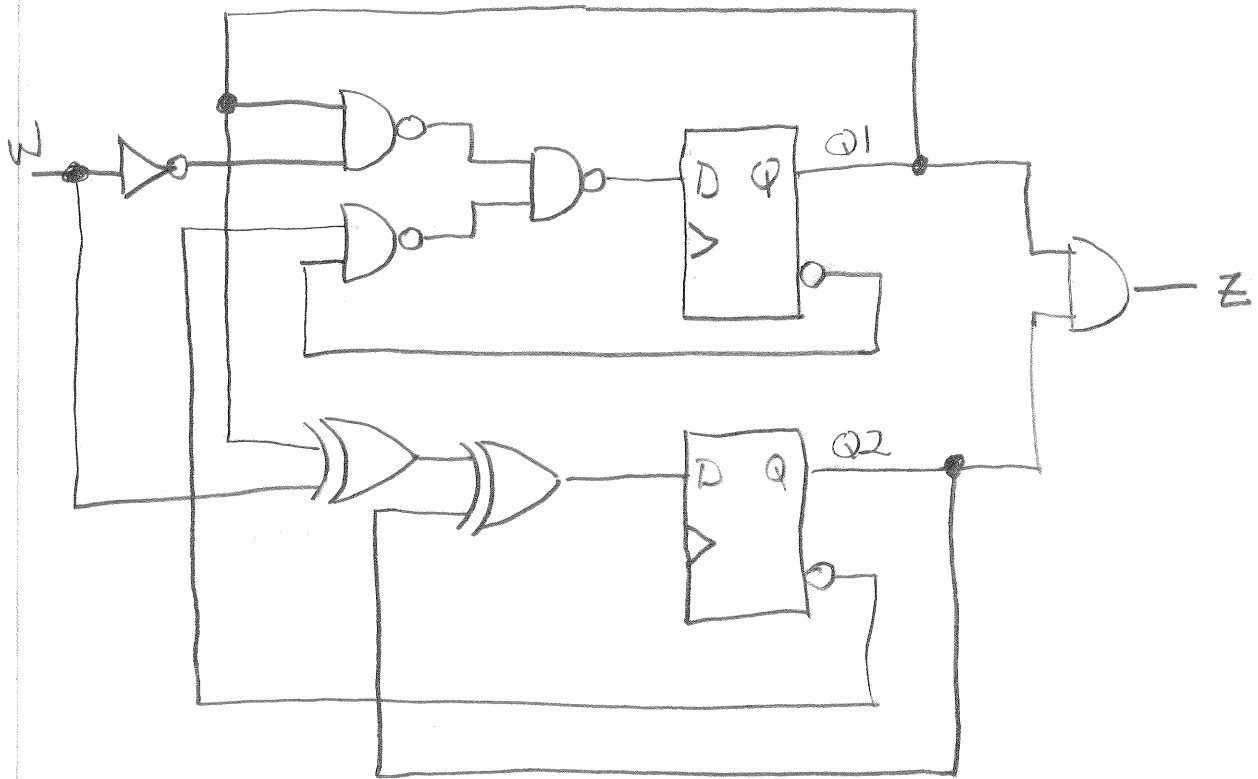
$$\begin{aligned}
 D2 &= Q1' \cdot Q2' \cdot W + Q1' \cdot Q2 \cdot W' + Q1 \cdot Q2 \cdot W \\
 &\quad + Q1 \cdot Q2' \cdot W' \\
 &= Q1' \cdot (Q2 \oplus W) + Q1 \cdot (Q2 \oplus W)' \\
 &= Q1 \oplus Q2 \oplus W
 \end{aligned}$$



As an exercise, change state encoding from binary to Gray code and repeat.